

Home Assignment 4

Marcus Malmquist, marmalm, 941022

December 4, 2016

1 Task 1

The scattering matrix \mathbf{S} of a four port is shown in (1).

$$\mathbf{S} = \begin{pmatrix} 0.2e^{j\frac{\pi}{2}} & 0.5e^{-j\frac{\pi}{4}} & 0.5e^{j\frac{\pi}{4}} & 0 \\ 0.5e^{-j\frac{\pi}{4}} & 0 & 0 & 0.5e^{j\frac{\pi}{4}} \\ 0.5e^{-j\frac{\pi}{4}} & 0 & 0 & 0.5e^{-j\frac{\pi}{4}} \\ 0 & 0.5e^{-j\frac{\pi}{4}} & 0.5e^{-j\frac{\pi}{4}} & 0 \end{pmatrix} \quad (1)$$

1.1 a

The circuit is lossless if \mathbf{S} is unitary. In order for \mathbf{S} to be unitary it has to be equal to its Hermitian conjugate (denoted \dagger) (2), which is not the case for \mathbf{S} as it is defined in (1).

$$\mathbf{S}\mathbf{S}^\dagger = \mathbf{I} \quad (2)$$

1.2 b

The circuit is lossless if \mathbf{S} is symmetric (3), which is not the case for \mathbf{S} as it is defined in (1).

$$\mathbf{S} = \mathbf{S}^T \quad (3)$$

1.3 c

The incident and reflected voltage waves are related through the scattering matrix as shown in (4)

$$\vec{V}^- = \mathbf{S}\vec{V}^+ \quad (4)$$

If the system is driven by a voltage wave incident at port 1 while all other ports are matched then

$$V_1^- = \mathbf{S}_{11}V_1^+ + \mathbf{S}_{1j} \overbrace{(1 - \delta_{i1})\mathbf{\Gamma} \underbrace{\mathbf{S}\vec{V}^+}_{\vec{V}^-}}^{\vec{V}'^+} = \mathbf{S}_{11}V_1^+ \quad (5)$$

where $\mathbf{\Gamma}_{ij} = \delta_{i1}\delta_{j1}$. Equation (5) implies that the reflection coefficient and return loss is

$$\Gamma = \mathbf{S}_{11} = 0.2e^{j\frac{\pi}{2}}, \quad (6a)$$

$$L_{\text{return}} = 10 \log_{10} |\mathbf{S}_{11}|^{-2} = 13.98 \text{ dB} \quad (6b)$$

1.4 c

If the system is driven by a voltage wave incident at port 3 or 4 and measurements are made at port 4 or 3 while all other ports are matched then the outgoing wave at the port is (7a) or (7b)

$$V_4^- = \mathbf{S}_{43} V_3^+, \quad (7a)$$

$$V_3^- = \mathbf{S}_{34} V_4^+ \quad (7b)$$

When the system is driven at port j and the output power is measured at port i then the losses between port i and j for this system can be calculated using (8).

$$L_{ij} = 10 \log_{10} \frac{P_{\text{in}}}{P_{\text{out}}} = 10 \log_{10} |\mathbf{S}_{ij}|^{-2} \quad (8)$$

When evaluating the losses between port 3 and 4 it is evident that $\mathbf{S}_{34} = \mathbf{S}_{43} = 0.5e^{-j\frac{\pi}{4}}$ so the loss is 6 dB both ways.

1.5 d

If the system is driven by a voltage wave incident at port 1 while port 3 is shorted and ports 2 and 4 are matched

$$V_1^- = \mathbf{S}_{11} V_1^+ + \mathbf{S}_{1j} \overbrace{(1 - \delta_{i1}) \mathbf{\Gamma} \mathbf{S} \vec{V}^+}^{\vec{V}'^+} = (\mathbf{S}_{11} - \mathbf{S}_{13} \mathbf{S}_{31}) V_1^+ \quad (9)$$

where $\mathbf{\Gamma}_{ij} = \delta_{i1}\delta_{j1} - \delta_{i3}\delta_{j3}$. Equation (9) implies that the reflection coefficient and return loss is

$$\Gamma = \mathbf{S}_{11} - \mathbf{S}_{13} \mathbf{S}_{31} = 0.2e^{j\frac{\pi}{2}} - 0.5^2 = -0.25 + j0.2, \quad (10a)$$

$$L_{\text{return}} = 10 \log_{10} |\mathbf{S}_{11} - \mathbf{S}_{13} \mathbf{S}_{31}|^{-2} = 9.89 \text{ dB}. \quad (10b)$$