



# Home assignment in microwave engineering


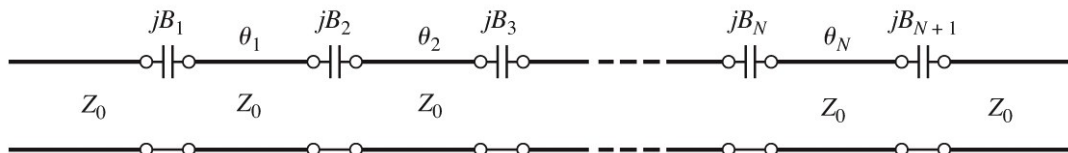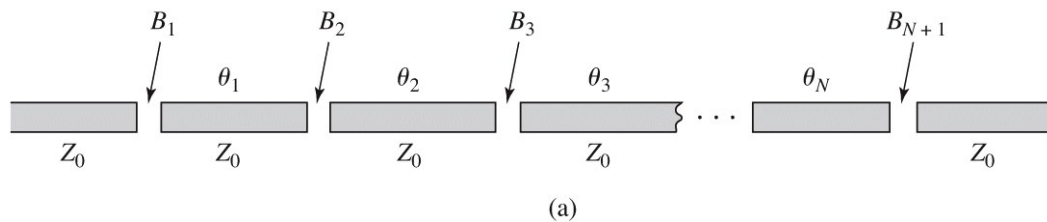
## Problem course week 6

Consider an infinite long filter based on capacitively coupled series resonators. It will act as a bandpass filter when each section is approximately  $\lambda/2$ . The line impedance is 50 ohm, electrical length is  $160^\circ$  at 2 GHz, and the gap capacitance is ca 0.5pF. Derive and plot the  $k$ - $\beta$  relationship (Brillouin diagram) assuming the filter consists of infinite number of unit cells in cascade (periodic). Discuss and compare with the 3-section example 8.9 in Pozar, which is based on a different synthesis approach. Hint! For a reciprocal network ( $AD-BC=I$ ), the propagation constant for a wave on an infinite long periodic structure can be derived from:

$$\cosh(\gamma d) = \frac{A+D}{2}, \text{ where } A \text{ and } D \text{ are } ABCD\text{-parameters of the unit cell.}$$



(1p)

Good Luck! / JS

## Home assignment in microwave Engineering: ferrite components

Derive the the S-parameters matrix for this 4 port ( $P_1$ ,  $P_2$ ,  $P_3$ ,  $P_4$  on the figure below) device using ferrites:

